

Homework (2)


Problem (1)

If the interconnection shown is valid, find the total power developed in the circuit.

If the interconnection is not valid, explain why.

$$P = VI = 50(5) + 10(5) - (40)(5) = 5(50+10-40) = 5(20) = 100 \text{ watts}$$

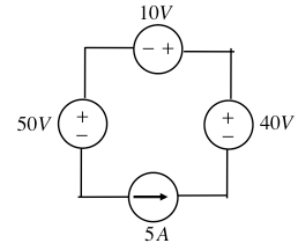The interconnection is valid because each node can hold the 5 amps, and this does not violate KVL or KCL.




Problem (2)

If the interconnection shown is valid, find the power developed by the current sources. If the interconnection is not valid, explain why.

The interconnection shown is valid because there are voltage sources connected in two different places in the circuit, therefore the currents will be different. None of Kirchhoff's Laws are violated.
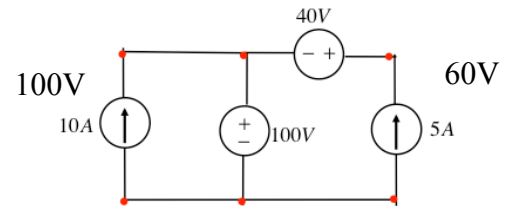
$$P = 10(100) + (100 + 40)(5) = 1700 \text{ Watts}$$




Problem (3)

If the interconnection shown is valid, find the total power developed in the circuit. If the interconnection is not valid, explain why.

The interconnection shown is valid because the voltage sources are able to carry the different currents.

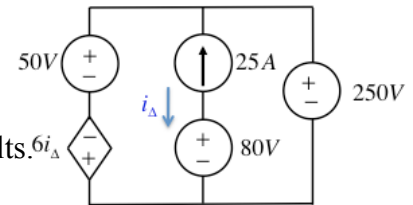
$i = -25$ amps since it is in the opposite direction of the independent current source, and $6 \cdot -25 = 125$ so that's the dependent voltage source. $6i = 125$ Volts.



Problem (4)

If, $v_o = 5V$, find the total power developed in the circuit shown.

Text

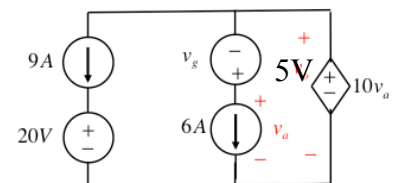

Problem (5)

- Is the interconnection shown valid? Explain.
- Can you find the total energy developed in the circuit? Explain

- No, the interconnection shown is not valid because the voltage sources in parallel are not the same value. KVL.
- No, you cannot find the total energy in the circuit because the circuit is invalid.

